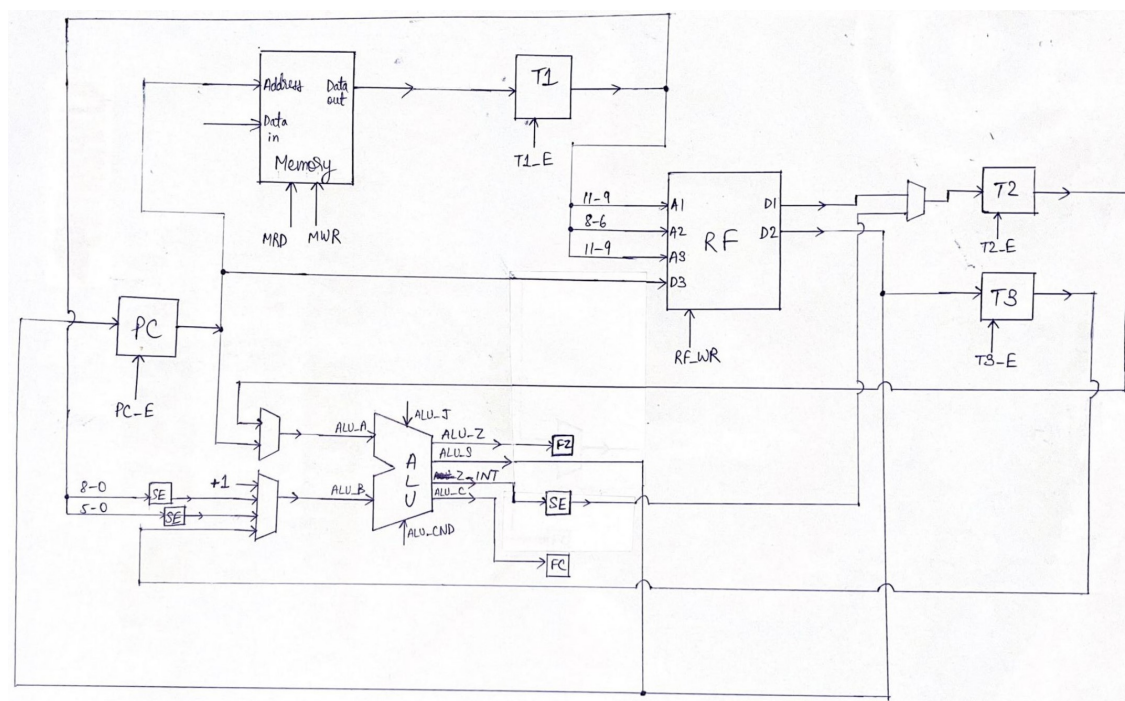


EE 224 Course Project : CPU

Atharva Kulkarni(210070047)
Harshit Raj(20d070033)
Shreyas Grampurohit(21d070029)
Varad Deshpande(21d070024)

9 Nov 2022

Data-flow



1

Inputs:

ALU_A: Takes 16-bit input

ALU_B: Takes 16-bit input

Registers storing the flags:

FC and FZ

These are connected to ALU_C and ALU_Z respectively.

Control Signals:

ALU_J: Takes 2-bit input. This specifies whether to perform addition, subtraction or NAND.

ALU_CND: Takes 2-bit input. This is used to find the new values to be updated to FZ and FC(may or may not be the same as the previous values in FZ and FC) based upon ALU_J(see table).

Outputs:

ALU_C: Outputs the carry flag to be put in the FZ register at the end of the clock cycle.

ALU_Z: Outputs the zero flag to be put in the FZ register at the end of the clock cycle. This may or may not be the same as Z.int.

ALU_S: Outputs sum, NAND, or the difference based on the bits provided in ALU_J.

Z.int: Evaluates to 1 when ALU_S is zero. Else, it evaluates to 0.

| ALU_J | Function |
|-------|-------------|
| 00 | Addition |
| 01 | NAND |
| 11 | Subtraction |

| ALU_J | ALU_CND | Output from ALU_C | Output from ALU_Z |
|---------------|---------------------------|---|--|
| 00 (Add) | 00 | Modified value of carry flag. | Modified value of zero flag. |
| 00 (Add) | 10 | Modified value of carry flag if input FC is 1. Same as the previous value in FC if FC is 0. | Modified value of zero flag if input FC is 1. Same as the previous value in FZ if FC is 0. |
| 00 (Add) | 01 | Modified value of carry flag if input FZ is 1. Same as the previous value in FC if FZ is 0. | Modified value of zero flag if input FZ is 1. Same as the previous value in FZ if FZ is 0 |
| 00 (Add) | 11 (Used for updating PC) | Same as the previous value in FC. | Same as the previous value in FZ. |
| 01 (NAND) | 00 | Same as the previous value in FC. | Modified value of zero flag. |
| 01 (NAND) | 10 | Same as the previous value in FC. | Modified value of zero flag if input FC is 1. Same as the previous value in FZ if FC is 0. |
| 01 (NAND) | 01 | Same as the previous value in FC. | Modified value of zero flag if input FZ is 1. Same as the previous value in FZ if FZ is 0. |
| 11 (Subtract) | xx | Same as the previous value in FC. | Same as the previous value in FZ. |

State Descriptions

(PC \equiv R7)

S_0 (Fetching instruction from memory)

| Data Transfer | Commands |
|-------------------------|----------|
| PC \rightarrow M.add | MDR |
| M.data \rightarrow T1 | T1.E |

S_1 (Updating PC)

| Data Transfer | Commands |
|-------------------------|-----------------------|
| PC \rightarrow ALU.A | PC.E |
| +1 \rightarrow ALU.B | ALU.J \leftarrow 00 |
| ALU.CND \leftarrow 11 | |
| ALU.S \rightarrow PC | |

S_2 (Reading operands)

| Data Transfer | Commands |
|-------------------------------|----------|
| $T1_{11-9} \rightarrow$ RF.A1 | T2.E |
| $T1_{8-6} \rightarrow$ RF.A2 | T3.E |
| RF.D1 \rightarrow T2 | |
| RF.D2 \rightarrow T3 | |

S_3 (Execution)

| Data Transfer | Commands |
|--------------------------------|---------------------------------|
| T2 \rightarrow ALU.A | T2.E |
| T3 \rightarrow ALU.B | ALU.J \leftarrow $T1_{14-13}$ |
| $T1_{1-0} \rightarrow$ ALU.CND | |
| ALU.S \rightarrow T2 | |
| ALU.C \rightarrow FC | |
| ALU.Z \rightarrow FZ | |

S_4 (Storing the output)

| Data Transfer | Commands |
|------------------------------|----------|
| T2 \rightarrow RF.D3 | RF.WR |
| $T1_{5-3} \rightarrow$ RF.A3 | |

S_5 (Reading operands (for ADI))

| Data Transfer | Commands |
|--|----------|
| $T1_{11-9} \rightarrow$ RF.A1 | T2.E |
| RF.D1 \rightarrow T2 | T3.E |
| $T1_{5-0} \rightarrow$ SE.6 \rightarrow T3 | |

S_6 (Evaluating condition for BEQ)

| Data Transfer | Commands |
|--|-------------------------------|
| T2 \rightarrow ALU_A T3 \rightarrow ALU_B Z_int \rightarrow SE_1 \rightarrow T2 ALU_CND \leftarrow 00 | ALU_J \leftarrow 11 T2_E |

S_7 (Updating PC in BEQ)

| Data Transfer | Commands |
|--|-------------------------------|
| PC \rightarrow ALU_A if($T2_0 == 0$) then $+1 \rightarrow$ ALU_B else $T1_{5-0} \rightarrow$ SE_6 \rightarrow ALU_B ALU_CND \leftarrow 11 ALU_S \rightarrow PC | ALU_J \leftarrow 00 PC_E |

S_8 (Storing PC into REG_A)

| Data Transfer | Commands |
|---|----------|
| $T1_{11-9} \rightarrow$ RF_A3 PC \rightarrow RF_D3 | RF_WR |

S_9 (Branching PC to the address PC + immediate)

| Data Transfer | Commands |
|--|-------------------------------|
| PC \rightarrow ALU_A $T1_{8-0} \rightarrow$ SE_9 \rightarrow ALU_B ALU_CND \leftarrow 11 ALU_S \rightarrow PC | ALU_J \leftarrow 00 PC_E |

S_{10} (Branching PC to the address in REG_B)

| Data Transfer | Commands |
|--|----------|
| $T1_{8-6} \rightarrow$ RF_A1 RF_D1 \rightarrow PC | PC_E |

S_{11} (Executing Load Higher Immediate)

| Data Transfer | Commands |
|--|----------|
| $T1_{11-9} \rightarrow$ RF_A3 $T1_{8-0} \rightarrow$ PZ_7 \rightarrow RF_D3 | RF_WR |

S_{12} (Computing address of the memory destination)

| Data Transfer | Commands |
|---|--|
| T3 \rightarrow ALU_A $T1_{5-0} \rightarrow$ SE_6 \rightarrow ALU_B ALU_S \rightarrow T3 | ALU_J \leftarrow 00 ALU_CND \leftarrow 11 T3_E |

S_{13} (Writing to the memory)

| Data Transfer | Commands |
|---|----------|
| T3 \rightarrow M_add T2 \rightarrow M_data | MWR |

S_{14} (Reading from memory)

| Data Transfer | Commands |
|-------------------------|----------|
| T3 \rightarrow M_add | MDR |
| M_data \rightarrow T2 | T2_E |

S_{15} (Writing to the register)

| Data Transfer | Commands |
|-------------------------------|----------|
| $T1_{11-9} \rightarrow$ RF_A3 | RF_WR |
| T2 \rightarrow RF_D3 | |

S_{16} (Initial step of SM and LM)

| Data Transfer | Commands |
|-------------------------------------|----------|
| (0000000000000000) \rightarrow T2 | T2_E |
| $T1_{11-9} \rightarrow$ RF_A2 | T3_E |
| RF_D2 \rightarrow T3 | |
| counter := int($T2_{2-0}$) | |

S_{17} (Looping step 1 of SM)

| Data Transfer | Commands |
|--------------------------------|-------------------------|
| T3 \rightarrow ALU_A | T3_E |
| +1 \rightarrow ALU_B | ALU_J \leftarrow 00 |
| if($T1_{counter} == 1$) then | ALU_CND \leftarrow 11 |
| { T3 \rightarrow M_add | MWR |
| $T2_{2-0} \rightarrow$ RF_A1 | |
| RF_D1 \rightarrow M_data | |
| ALU_S \rightarrow T3 } | |

S_{18} (Updating counter variable (Looping step 2 of SM and LM))

| Data Transfer | Commands |
|---|-------------------------|
| counter (converted to 16 bit) \rightarrow ALU_A | ALU_J \leftarrow 00 |
| 1 bit \rightarrow ALU_B | ALU_CND \leftarrow 11 |
| ALU_S \rightarrow counter | |

S_{19} (Looping step 1 of LM)

| Data Transfer | Commands |
|---|-------------------------|
| $T1_{counter} \rightarrow$ RF_WR | T3_E |
| T3 \rightarrow M_add | ALU_J \leftarrow 00 |
| M_data \rightarrow RF_D3 | ALU_CND \leftarrow 11 |
| $T2_{2-0} \rightarrow$ RF_A3 | MDR |
| T3 \rightarrow ALU_A | |
| +1 \rightarrow ALU_B | |
| if($T1_{counter} == 1$) then ALU_S \rightarrow T3 | |

Instructions with their State Diagrams and Control Signals

| Instruction | State flow |
|-------------|--|
| ADD | $S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$ |
| ADC | $S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$ |
| ADZ | $S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$ |
| ADI | $S_0 \rightarrow S_1 \rightarrow S_5 \rightarrow S_3 \rightarrow S_4$ |
| NDU | $S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$ |
| NDC | $S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$ |
| NDZ | $S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$ |
| LHI | $S_0 \rightarrow S_1 \rightarrow S_{11}$ |
| LW | $S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_{12} \rightarrow S_{14} \rightarrow S_{15}$ |
| SW | $S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_{12} \rightarrow S_{13}$ |
| SM | $S_0 \rightarrow S_1 \rightarrow S_{16} \rightarrow S_{17} S_{18}$ |
| LM | $S_0 \rightarrow S_1 \rightarrow S_{16} \rightarrow S_{19} S_{18}$ |
| BEQ | $S_0 \rightarrow S_2 \rightarrow S_6 \rightarrow S_7$ |
| JAL | $S_0 \rightarrow S_8 \rightarrow S_9$ |
| JLR | $S_0 \rightarrow S_8 \rightarrow S_{10}$ |

 


Figure 1: State Transition Diagram