

# EE 224 Course Project : CPU

Atharva Kulkarni(210070047)  
Harshit Raj(20d070033)  
Shreyas Grampurohit(21d070029)  
Varad Deshpande(21d070024)

9 Nov 2022

## State Descriptions

$S_0$  (Fetching instruction from memory)

Data Transfer	Commands
PC $\rightarrow$ M.add	MDR
M.data $\rightarrow$ T1	T1.E

$S_1$  (Updating PC)

Data Transfer	Commands
PC $\rightarrow$ ALU_A	PC.E
+1 $\rightarrow$ ALU_B	ALU.J
ALU_CND $\leftarrow$ 11	
ALU_S $\rightarrow$ PC	

$S_2$  (Reading operands)

Data Transfer	Commands
$T1_{11-9} \rightarrow$ RF_A1	T2.E
$T1_{8-6} \rightarrow$ RF_A2	T3.E
RF_D1 $\rightarrow$ T2	
RF_D2 $\rightarrow$ T3	

**$S_3$  (Execution)**

Data Transfer	Commands
T2 $\rightarrow$ ALU_A	T2_E
T3 $\rightarrow$ ALU_B	ALU_J
$T1_{1-0} \rightarrow$ ALU_CND	
ALU_S $\rightarrow$ T2	
ALU_C $\rightarrow$ FC	
ALU_Z $\rightarrow$ FZ	

**$S_4$  (Storing the output)**

Data Transfer	Commands
T2 $\rightarrow$ RF_D3	RF_WE
$T1_{5-3} \rightarrow$ RF_A3	

**$S_5$  (Reading operands (for ADI))**

Data Transfer	Commands
$T1_{11-9} \rightarrow$ RF_A1	T2_E
RF_D1 $\rightarrow$ T2	T3_E
$T1_{5-0} \rightarrow$ SE_6 $\rightarrow$ T3	

**$S_6$  (Checking whether the two operands are equal, and storing zero flag into T2 (without changing FZ))**

Data Transfer	Commands
T2 $\rightarrow$ ALU_A	ALU_J
T3 $\rightarrow$ ALU_B	T2_E
ALU_C $\rightarrow$ SE_2 $\rightarrow$ T2	
ALU_CND $\leftarrow$ 00	

**$S_7$  (Updating PC if BEQ)**

Data Transfer	Commands
PC $\rightarrow$ ALU_A	ALU_J
$T1 \rightarrow$ SE_10 $\rightarrow$ ALU_B	PC_E
ALU_CND $\leftarrow$ 11	
if( $T2_0 == 0$ ) then ALU_C $\rightarrow$ PC	
else PC $\rightarrow$ PC	

**$S_8$  (Storing PC into REG\_A)**

Data Transfer	Commands
$T1_{11-9} \rightarrow$ RF_A3	RF_WE
PC $\rightarrow$ RF_D3	

$S_9$  (Branching PC to the address PC + immediate)

Data Transfer	Commands
PC $\rightarrow$ ALU_A $T1_{8-0} \rightarrow$ SE_9 $\rightarrow$ ALU_B ALU_CND $\leftarrow$ 11 ALU_S $\rightarrow$ PC	ALU_J

$S_{10}$  (Branching PC to the address in REG\_B)

Data Transfer	Commands
$T1_{8-6} \rightarrow$ RF_A1 RF_D1 $\rightarrow$ PC	PC_E

$S_{11}$  (Executing Load Higher Immediate)

Data Transfer	Commands
$T1_{11-9} \rightarrow$ RF_A3 $T1_{11-9} \rightarrow$ PZ_7 $\rightarrow$ RF_D3	RF_WE

$S_{12}$  (Executing Load Higher Immediate)

Data Transfer	Commands
$T1_{11-9} \rightarrow$ RF_A3 $T1_{11-9} \rightarrow$ PZ_7 $\rightarrow$ RF_D3	RF_WE

$S_{14}$  (Computing address of the memory destination)

Data Transfer	Commands
T3 $\rightarrow$ ALU_A $T1_{5-0} \rightarrow$ SE_16 $\rightarrow$ ALU_B ALU_C $\rightarrow$ T3	ALU_CND T3_E

$S_{15}$  (Writing to the memory)

Data Transfer	Commands
T3 $\rightarrow$ M_add T2 $\rightarrow$ M_data	MWR

$S_{16}$  (Computing address of the memory destination)

Data Transfer	Commands
T3 $\rightarrow$ ALU_A $T1_{5-0} \rightarrow$ SE_16 $\rightarrow$ ALU_B ALU_C $\rightarrow$ T3	ALU_CND T3_E ALU_CND

$S_{17}$  (Reading from memory)

Data Transfer	Commands
T3 $\rightarrow$ M_add	MDR
T2 $\rightarrow$ M_data	T2_E

$S_{18}$  (Writing to the register)

Data Transfer	Commands
$T1_{11-9} \rightarrow$ RF_A3 T2 $\rightarrow$ RF_D3	RF_WE

$S_{19}$  (Initial step of SM)

Data Transfer	Commands
(0000000000000000) $\rightarrow$ T2 $T1_{11-9} \rightarrow$ RF_A2 RF_D2 $\rightarrow$ T3	T2_WE T3_E

$S_{20}$  (Looping step 1 of SM)

Data Transfer	Commands
counter := int( $T2_{2-0}$ ) if( $T1_{counter}=1$ ) then T3 $\rightarrow$ RF_D1 $\rightarrow$ M_data $T2_{2-0} \rightarrow$ RF_A1	MWR

$S_{21}$  (Looping step 2 of SM)

Data Transfer	Commands
T3 $\rightarrow$ ALU_A 1 $\rightarrow$ ALU_B if( $T1_{counter}=1$ ) then ALU_C $\rightarrow$ T3	T3_E ADD

$S_{22}$  (Looping step 3 of SM)

Data Transfer	Commands
T2 $\rightarrow$ ALU_A 1 $\rightarrow$ ALU_B ALU_C $\rightarrow$ T2	ADD T2_E

$S_{23}$  (Initial step of LM)

Data Transfer	Commands
(0000000000000000) $\rightarrow$ T2 $T1_{11-9} \rightarrow$ RF_A2 RF_D3 $\rightarrow$ T3	T2_WE T3_E

$S_{24}$  (Looping step 1 of LM)

Data Transfer	Commands
counter := int( $T2_{2-0}$ )	MDR
$T1_{counter} \rightarrow \text{RF\_WR}$	MDR
$T3 \rightarrow \text{M\_add}$	
$\text{M\_data} \rightarrow \text{RF\_D3}$	
$T2_{2-0} \rightarrow \text{RF\_A3}$	

$S_{25}$  (Looping step 2 of LM)

Data Transfer	Commands
$T3 \rightarrow \text{ALU\_A}$	T3.E
$1 \rightarrow \text{ALU\_B}$	ADD
if( $T1_{counter} == 1$ ) then $\text{ALU\_C} \rightarrow T3$	

$S_{26}$  (Looping step 3 of LM)

Data Transfer	Commands
$T2 \rightarrow \text{ALU\_A}$	ADD
$1 \rightarrow \text{ALU\_B}$	T2.E
$\text{ALU\_C} \rightarrow T2$	

## Instructions with their State Diagrams and Control Signals

Instruction	State flow	Control
ADD	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$	
ADC	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$	
ADZ	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$	
ADI	$S_0 \rightarrow S_1 \rightarrow S_5 \rightarrow S_3 \rightarrow S_4$	