



EE 224 Course Project : CPU

Atharva Kulkarni(210070047)
Harshit Raj(20d070033)
Shreyas Grampurohit(21d070029)
Varad Deshpande(21d070024)

9 Nov 2022

ALU:

Data-flow

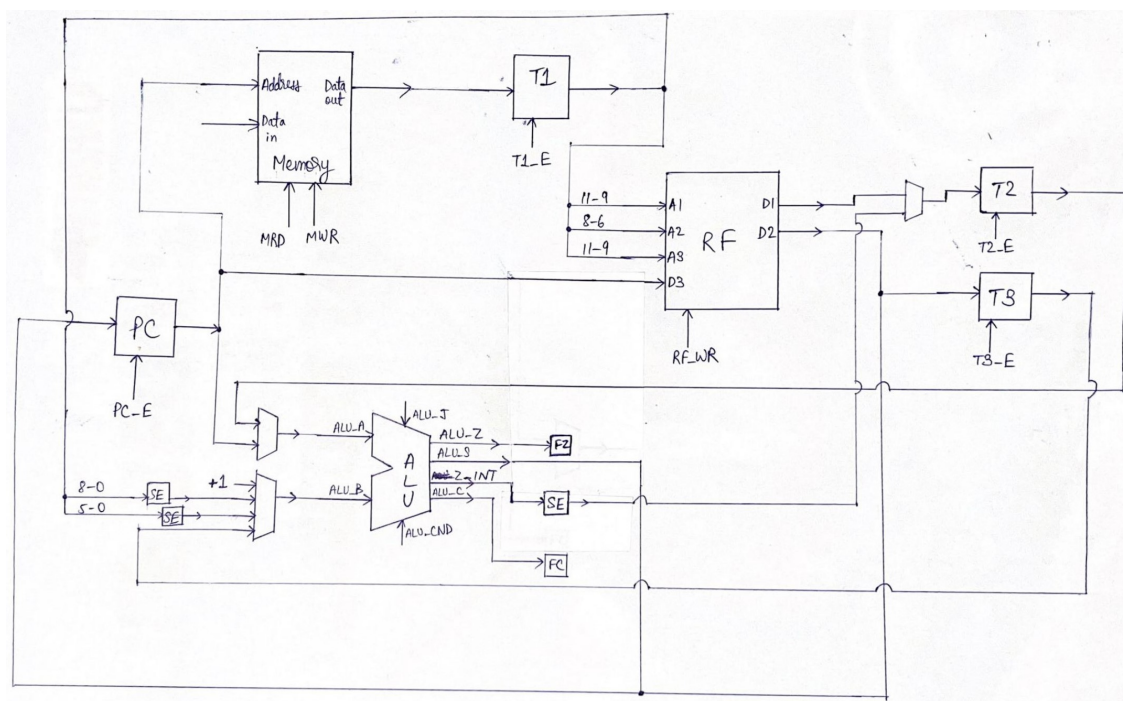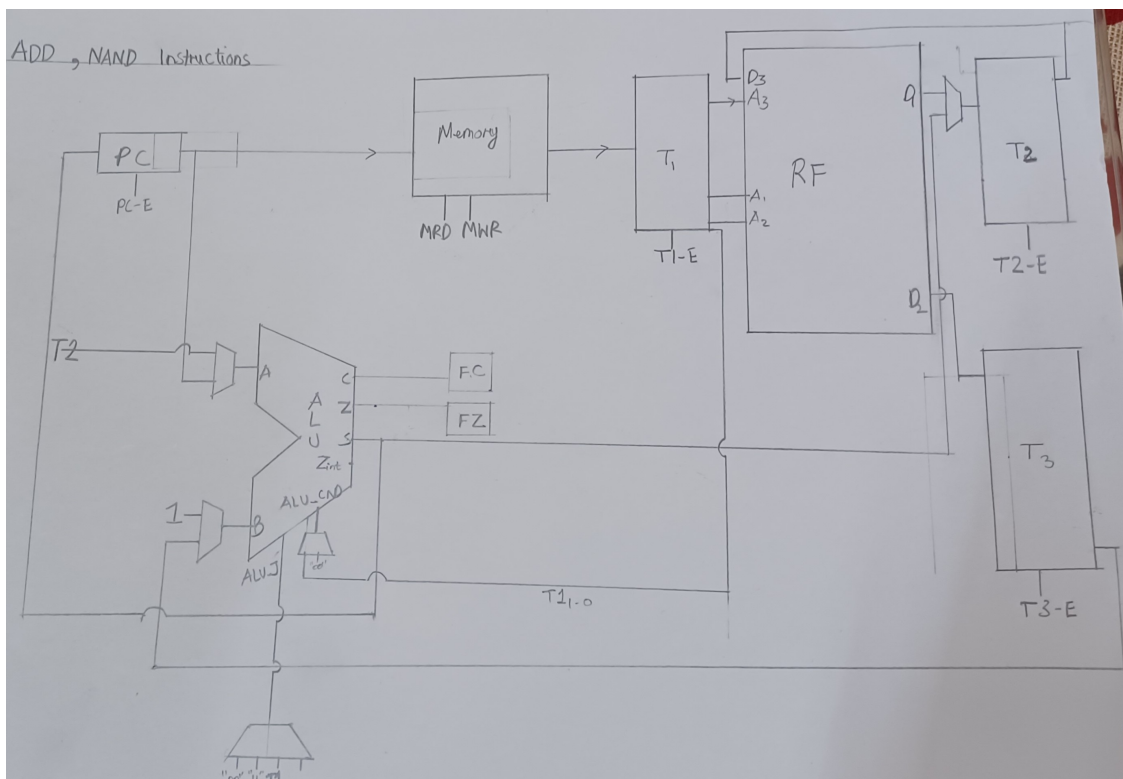

We have separated data-flow diagrams for ADD, NAND instructions from other instructions for simplicity.

Inputs:

ALU_A: Takes 3-bit input

ALU_B: Takes 3-bit input

Registers storing the flags:

FC and FZ

These are connected to ALU_C and ALU_Z respectively.

Control Signals:

ALU_J: Takes 2-bit input. This specifies whether to perform addition, subtraction or NAND.

ALU_CND: Takes 2-bit input. This is used to find the new values to be updated to FZ and FC(may or may not be the same as the previous values in FZ and FC) based upon ALU_J(see table).

Outputs:

ALU_C: Outputs the carry flag to be put in the FZ register at the end of the clock cycle.

ALU_Z: Outputs the zero flag to be put in the FZ register at the end of the clock cycle. This may or may not be the same as Z.int.

ALU_S: Outputs sum, NAND, or the difference based on the bits provided in ALU_J.

Z.int: Evaluates to 1 when ALU_S is zero. Else, it evaluates to 0.

ALU_J	Function
00	Addition
01	NAND
11	Subtraction

ALU_J	ALU_CND	Output from ALU_C	Output from ALU_Z
00 (Add)	00	Modified value of carry flag.	Modified value of zero flag.
00 (Add)	10	Modified value of carry flag if input FC is 1. Same as the previous value in FC if FC is 0.	Modified value of zero flag if input FC is 1. Same as the previous value in FZ if FC is 0.
00 (Add)	01	Modified value of carry flag if input FZ is 1. Same as the previous value in FC if FZ is 0.	Modified value of zero flag if input FZ is 1. Same as the previous value in FZ if FZ is 0
00 (Add)	11 (Used for updating PC)	Same as the previous value in FC.	Same as the previous value in FZ.
01 (NAND)	00	Same as the previous value in FC.	Modified value of zero flag.
01 (NAND)	10	Same as the previous value in FC.	Modified value of zero flag if input FC is 1. Same as the previous value in FZ if FC is 0.
01 (NAND)	01	Same as the previous value in FC.	Modified value of zero flag if input FZ is 1. Same as the previous value in FZ if FZ is 0.
11 (Subtract)	xx	Same as the previous value in FC.	Same as the previous value in FZ.

State Descriptions

(PC \equiv R7)

S_0 (Fetching instruction from memory)

Data Transfer	Commands
PC \rightarrow M.add	MDR
M.data \rightarrow T1	T1.E

S_1 (Updating PC)

Data Transfer	Commands
PC \rightarrow ALU.A	PC.E
+1 \rightarrow ALU.B	ALU.J \leftarrow 00
ALU.CND \leftarrow 11	
ALU.S \rightarrow PC	

S_2 (Reading operands)

Data Transfer	Commands
$T1_{11-9} \rightarrow$ RF.A1	T2.E
$T1_{8-6} \rightarrow$ RF.A2	T3.E
RF.D1 \rightarrow T2	
RF.D2 \rightarrow T3	

S_3 (Execution)

Data Transfer	Commands
T2 \rightarrow ALU.A	T2.E
T3 \rightarrow ALU.B	ALU.J \leftarrow $T1_{14-13}$
$T1_{1-0} \rightarrow$ ALU.CND	
ALU.S \rightarrow T2	
ALU.C \rightarrow FC	
ALU.Z \rightarrow FZ	

S_4 (Storing the output)

Data Transfer	Commands
T2 \rightarrow RF.D3	RF.WR
$T1_{8-6} \rightarrow$ RF.A3	

S_5 (Reading operands (for ADI))

Data Transfer	Commands
$T1_{11-9} \rightarrow$ RF.A1	T2.E
RF.D1 \rightarrow T2	T3.E
$T1_{5-0} \rightarrow$ SE.6 \rightarrow T3	

S_6 (Evaluating condition for BEQ)

Data Transfer	Commands
T2 \rightarrow ALU_A	ALU_J \leftarrow 11
T3 \rightarrow ALU_B	T2_E
Z_int \rightarrow SE_1 \rightarrow T2	
ALU_CND \leftarrow 00	

S_7 (Updating PC in BEQ)

Data Transfer	Commands
PC \rightarrow ALU_A	ALU_J \leftarrow 00
if($T2_0 == 0$) then $+1 \rightarrow$ ALU_B	PC_E
else $T1 \rightarrow$ SE_10 \rightarrow ALU_B	
ALU_CND \leftarrow 11	
ALU_S \rightarrow PC	

S_8 (Storing PC into REG_A)

Data Transfer	Commands
$T1_{11-9} \rightarrow$ RF_A3	RF_WR
PC \rightarrow RF_D3	

S_9 (Branching PC to the address PC + immediate)

Data Transfer	Commands
PC \rightarrow ALU_A	ALU_J
$T1_{8-0} \rightarrow$ SE_9 \rightarrow ALU_B	
ALU_CND \leftarrow 11	
ALU_S \rightarrow PC	

S_{10} (Branching PC to the address in REG_B)

Data Transfer	Commands
$T1_{8-6} \rightarrow$ RF_A1	PC_E
RF_D1 \rightarrow PC	

S_{11} (Executing Load Higher Immediate)

Data Transfer	Commands
$T1_{11-9} \rightarrow$ RF_A3	RF_WR
$T1_{11-9} \rightarrow$ PZ_7 \rightarrow RF_D3	

S_{12} (Computing address of the memory destination)

Data Transfer	Commands
T3 \rightarrow ALU_A	ALU_J \leftarrow 00
$T1_{5-0} \rightarrow$ SE_16 \rightarrow ALU_B	T3_E
ALU_S \rightarrow T3	

S_{13} (Writing to the memory)

Data Transfer	Commands
T3 \rightarrow M_add	MWR
T2 \rightarrow M_data	

S_{14} (Reading from memory)

Data Transfer	Commands
$T3 \rightarrow M_add$	MDR
$M_data \rightarrow T2$	T2_E

S_{15} (Writing to the register)

Data Transfer	Commands
$T1_{11-9} \rightarrow RF_A3$	RF_WR
$T2 \rightarrow RF_D3$	

S_{16} (Initial step of SM)

Data Transfer	Commands
$(0000000000000000) \rightarrow T2$	T2_E
$T1_{11-9} \rightarrow RF_A2$	T3_E
$RF_D2 \rightarrow T3$	

S_{17} (Looping step 1 of SM)

Data Transfer	Commands
counter := int($T2_{2-0}$)	MWR
$T3 \rightarrow ALU_A$	T3_E
$+1 \rightarrow ALU_B$	$ALU_J \leftarrow 00$
if($T1_{counter} == 1$) then	
{ $T3 \rightarrow M_add$	
$T2_{2-0} \rightarrow RF_A1$	
$RF_D1 \rightarrow M_data$	
$ALU_S \rightarrow T3$ }	

S_{18} (Looping step 2 of SM)

Data Transfer	Commands
$T2 \rightarrow ALU_A$	$ALU_J \leftarrow 00$
1 bit $\rightarrow ALU_B$	T2_E
$ALU_C \rightarrow T2$	

S_{19} (Initial step of LM)

Data Transfer	Commands
$(0000000000000000) \rightarrow T2$	T2_E
$T1_{11-9} \rightarrow RF_A3$	T3_E
$RF_D3 \rightarrow T3$	

S_{20} (Looping step 1 of LM)

Data Transfer	Commands
$\text{counter} := \text{int}(T2_{2-0})$ $T1_{\text{counter}} \rightarrow \text{RF_WR}$ $T3 \rightarrow \text{M_add}$ $\text{M_data} \rightarrow \text{RF_D3}$ $T2_{2-0} \rightarrow \text{RF_A3}$ $T3 \rightarrow \text{ALU_A}$ $+1 \rightarrow \text{ALU_B}$ $\text{ALU_CND} \leftarrow 00$ $\text{if}(T1_{\text{counter}}==1) \text{ then } \text{ALU_S} \rightarrow T3$	MDR $T3_E$ $\text{ALU_J} \leftarrow 00$

S_{21} (Looping step 2 of LM)

Data Transfer	Commands
$T2 \rightarrow \text{ALU_A}$ $1 \text{ bit} \rightarrow \text{ALU_B}$ $\text{ALU_S} \rightarrow T2$	$\text{ALU_J} \leftarrow 00$ $T2_E$

Instructions with their State Diagrams and Control Signals

Instruction	State flow
ADD	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$
ADC	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$
ADZ	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$
ADI	$S_0 \rightarrow S_1 \rightarrow S_5 \rightarrow S_3 \rightarrow S_4$
NDU	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$
NDC	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$
NDZ	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow S_4$
LHI	$S_0 \rightarrow S_1 \rightarrow S_{11}$
LW	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_{12} \rightarrow S_{14} \rightarrow S_{15}$
SW	$S_0 \rightarrow S_1 \rightarrow S_2 \rightarrow S_{12} \rightarrow S_{13}$
SM	$S_0 \rightarrow S_1 \rightarrow S_{16} \rightarrow S_{17} S_{18}$
LM	$S_0 \rightarrow S_1 \rightarrow S_{19} \rightarrow S_{20} S_{21}$
BEQ	$S_0 \rightarrow S_2 \rightarrow S_6 \rightarrow S_7$
JAL	$S_0 \rightarrow S_8 \rightarrow S_9$
JLR	$S_0 \rightarrow S_8 \rightarrow S_{10}$

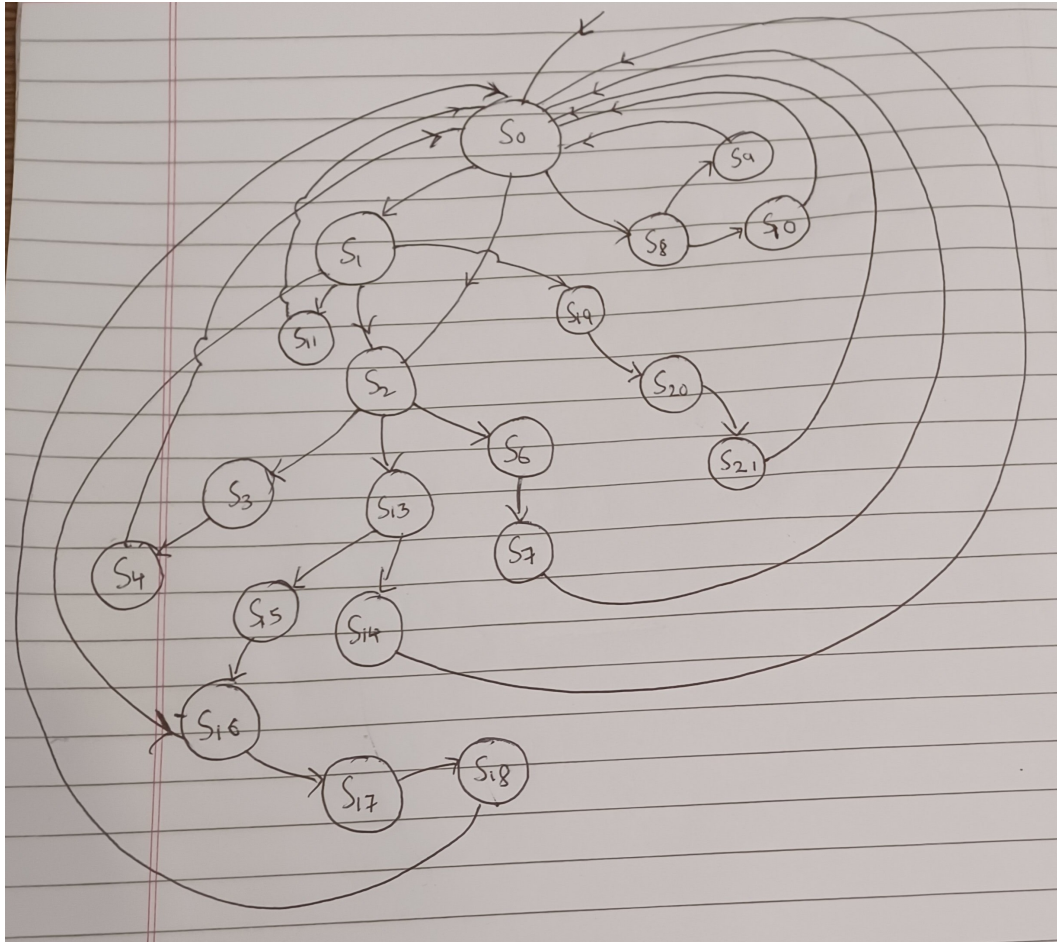


Figure 1: State Transition Diagram